

Week 4
Let's Build a Computer!

Aditya (@nebu)



Outline

Combinational Logic


Feedback and FSMs

Building a Computer



Why Are We Doing This?

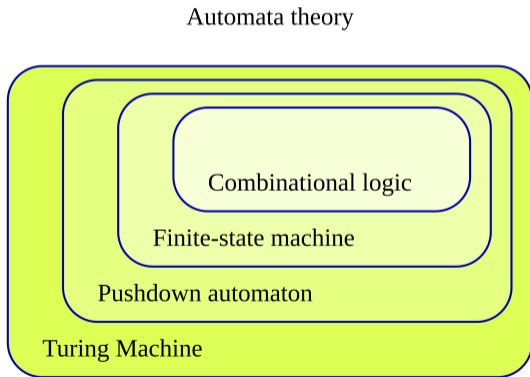- Understanding automata theory means understanding, in part, what the things in this figure mean:



Why Are We Doing This?

- Understanding automata theory means understanding, in part, what the things in the figure on the previous slide mean.
- Teaches an application of what we're learning.
- Shows how general and useful the ideas we're covering are. (@Hassam compilers soon? 🙄)
- Is very rewarding since computers are everywhere.




Section 1

Combinational Logic



NOT Gate

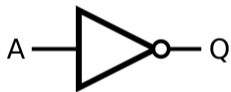

A	$Q = \overline{A}$
0	1
1	0



AND Gate



A	B	$Q = AB$
0	0	0
0	1	0
1	0	0
1	1	1



OR Gate



A	B	$Q = A + B$
0	0	0
0	1	1
1	0	1
1	1	1



That's It!*

- AND, OR, and NOT are functionally complete.
- This means we can turn any “Boolean” function into one that's made up of **only** ANDs, ORs, and NOTs.



Constructive Proof

A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



Constructive Proof

A	B	C	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Q = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C} + ABC$$

This works because we “look for” all combinations of A, B, and C that’ll make Q high. If any of those combinations are high, Q is high.



Questions?



Questions!


Write F as an expression of A, B, and S.

S	A	B	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1



Solution

$$F = \bar{S}A + SB$$

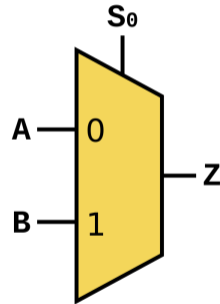

Takeaways Before We Move On

- We can now map any input bits to output bits.
- You can build any Boolean function using only AND, OR, and NOT.
- Using this knowledge, you can build adders, multipliers, decoders, priority MUXes...whatever you want really.



Section 2

Feedback and FSMs




A Fly in the Soup

- When I said you could build anything you wanted, what did I miss?
- **Storage.**
- Any ideas?



Consider This: No Longer Combinational

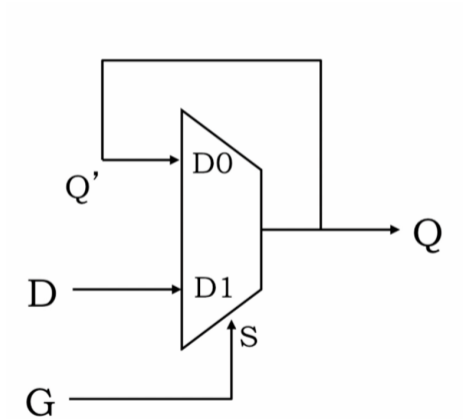

That's a Latch

It's rarely used as a memory element — can you guess why?


Latches are level triggered.



To Explain This, Let's Talk About Cars




Timing is Key, Or Else...

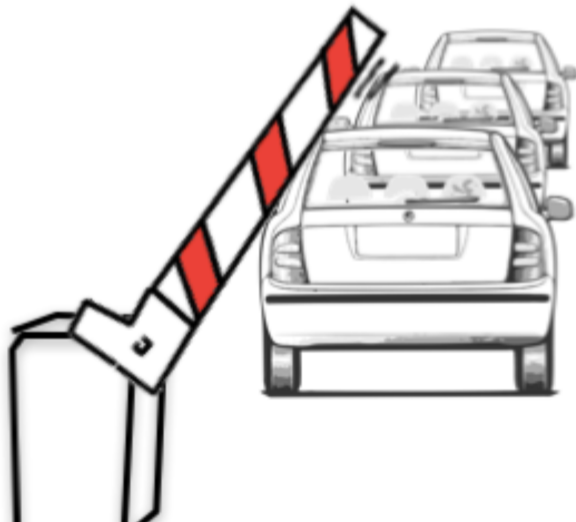


Any ideas?



Use Two Barriers!

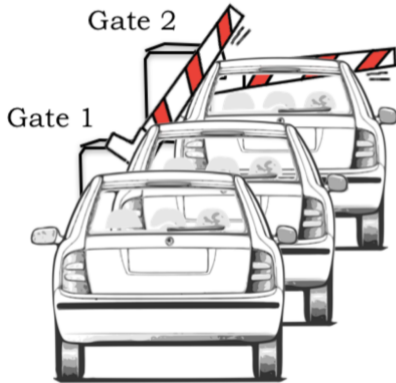

Gate 1: open
Gate 2: closed

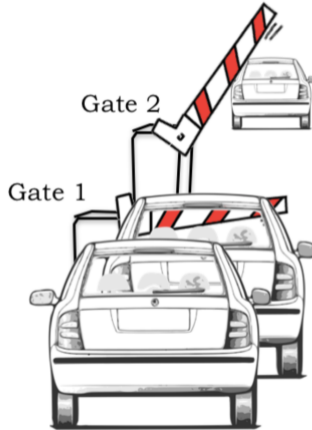

Gate 1: closed
Gate 2: open




How Does This Help?

- Timing is now easy — we just need to push one switch to swap the states of the barriers.
- Actually making two barriers in hardware isn't very tricky...



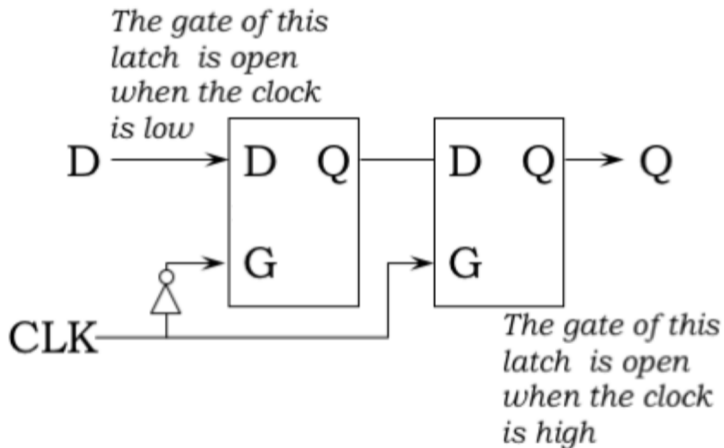
D Flip Flop/ D Register...Finally a Nice Storage Element!



Who Flips the Switch?

What we really need is a **low to high transition**, to load data correctly into our flip flop.

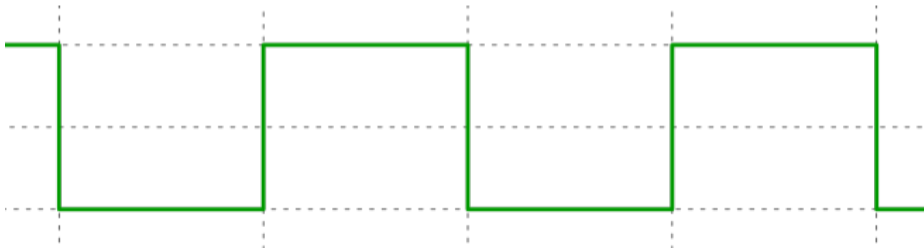We use an alternating signal, called a clock, to give us these transitions at regular intervals.



Synchronous Digital Logic

A synchronous digital circuit is made up of flip flops/latches and combinational logic, all run by a single clock.



Questions?




Questions!

You're given a D flip flop, a NOT gate, and a clock signal. Make a circuit that, on every 0 to 1 transition of the clock, inverts the value stored in the flip flop. You may assume the flip flop is initialized with a valid value.

Hint: Think about when the flip flop loads data, and what data it should load.




Solution

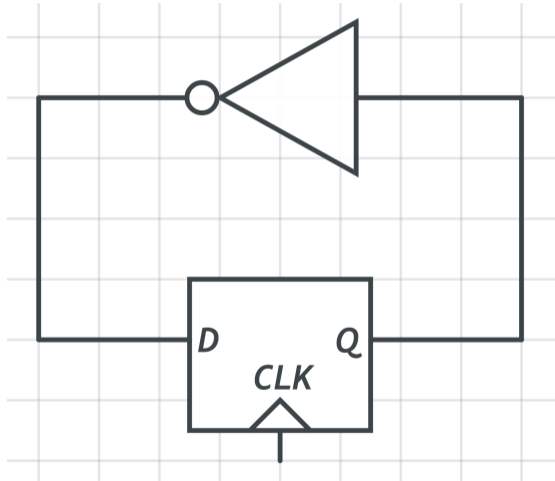

We Can Now Build FSMs!

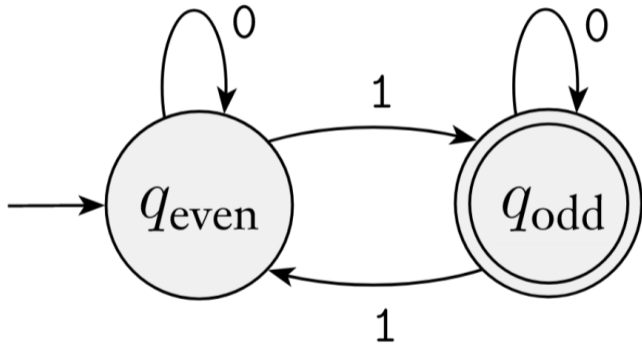Recall that a DFA is simply something like:




Let's build something similar¹ using our synchronous logic.

¹Formally, a finite state transducer.



What is an FSM, *Really*

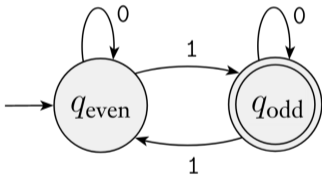

- An input alphabet: $\{0, 1\}$
- A bunch of states: $\{q_{\text{even}}, q_{\text{odd}}\}$
- An initial state: q_{even}
- A state transition function:

State	Input	Next State
q_{even}	0	q_{even}
q_{even}	1	q_{odd}
q_{odd}	0	q_{odd}
q_{odd}	1	q_{even}



Now, Let's Make it in Hardware

- An input alphabet: $\{0, 1\}$
- A bunch of states: $\{q_{\text{even}}, q_{\text{odd}}\}$
- An initial state: q_{even}
- A state transition function:


State	Input	Next State
q_{even}	0	q_{even}
q_{even}	1	q_{odd}
q_{odd}	0	q_{odd}
q_{odd}	1	q_{even}

- An input alphabet: $\{0, 1\}$
- A bunch of states: use a flip flop, $(q_{\text{even}}, q_{\text{odd}}) = (0, 1)$.
- An initial state: initialize the flip flop to 0.
- A state transition function:

State	Input	Next State
0	0	0
0	1	1
1	0	1
1	1	0



Our Final Hardware FSM Is

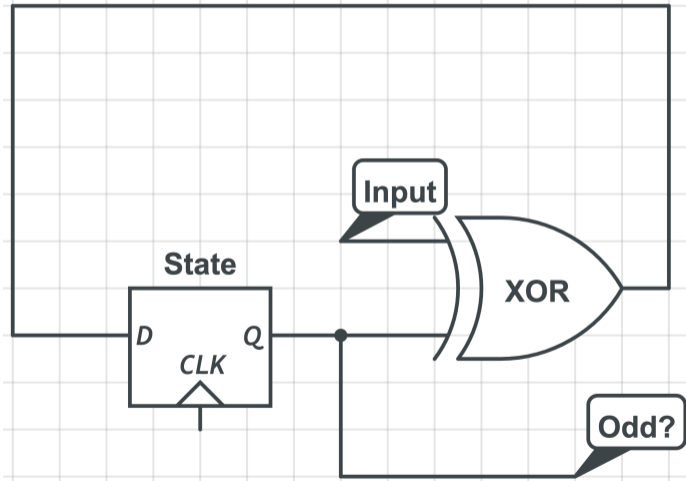


Hardware FSMs Also Have Outputs

- An output alphabet
- An output function that maps states to outputs



Generalized (Moore) FSM Architecture

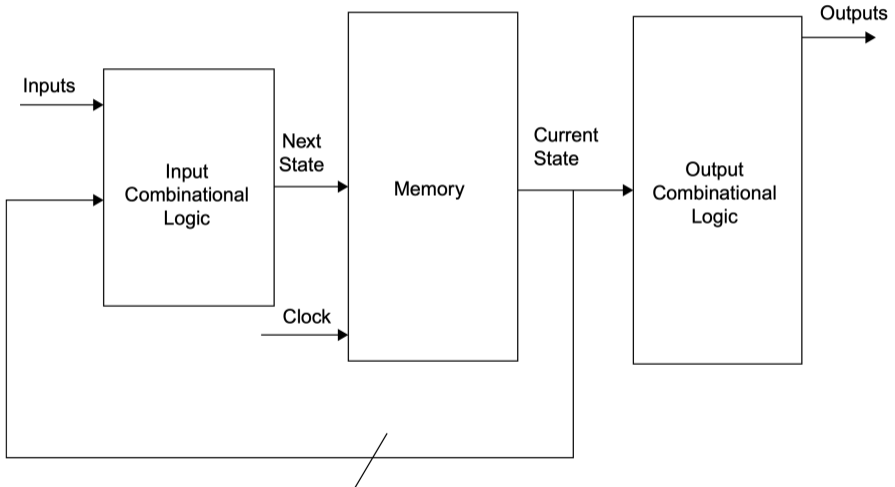

Questions?



Questions!

Design in hardware an FSM that detects non-overlapping sequences of the string 101. (Your input alphabet is $\{0, 1\}$.)



Section 3

Building a Computer



What is a Computer?


According to Wikipedia...

A computer is a digital electronic machine that can be programmed to carry out sequences of arithmetic or logical operations (computation) automatically.

Surprisingly accurate description — of a CPU.



Von Neumann Architecture

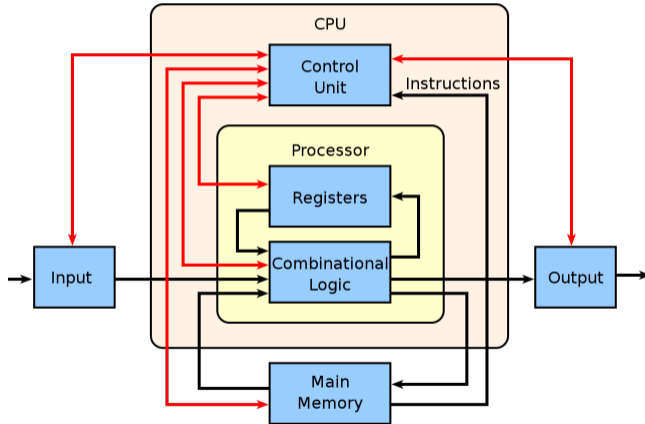

A CPU Has

- **Memory:** We'll assume it's random access. The CPU can read/write values from here at will.
- **Registers:** a bunch of flip flops where it stores values that it's currently operating on.
- **Combinational logic** to “compute” things: adders, logical units, etc. whose inputs and outputs are the registers.
- **Instructions:** Stored in the memory, (logically) executed one after another.
- **Control Unit:** Orchestrates the whole thing.



The Control Unit Is

A giant FSM that does the following things:

- **Fetch:** Gets an “instruction” from memory.
- **Decode:** Figures out what to do according to the instruction.
- **Execute:** Actually do the instruction. Once it’s done, go decode the next instruction in memory — increment the program counter.





Instructions

What can the CPU do?

- **ADD:** Takes two registers, adds them, puts the sum in a register. Set condition codes.
- **AND:** Takes two registers, ANDs them, puts the result in a register. Set condition codes.
- **NOT:** Takes a register, NOTs it, puts the result in a register. Set condition codes.
- **BR:** Depending on “condition codes”, move the program counter to the location specified.
- **JMP:** Move the program counter to the address specified.
- **LDR:** Load the contents of a memory address into a register.
- **STR:** Store the contents of a register into a memory address.



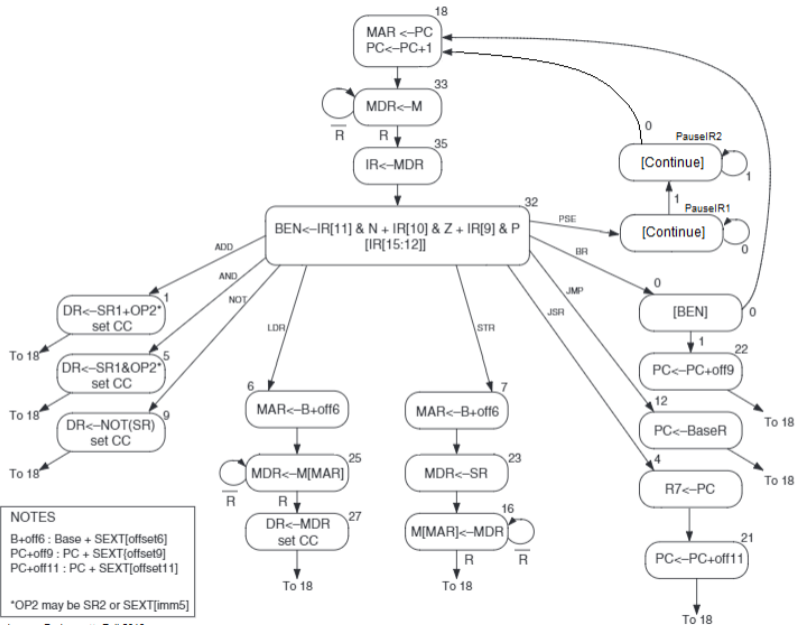

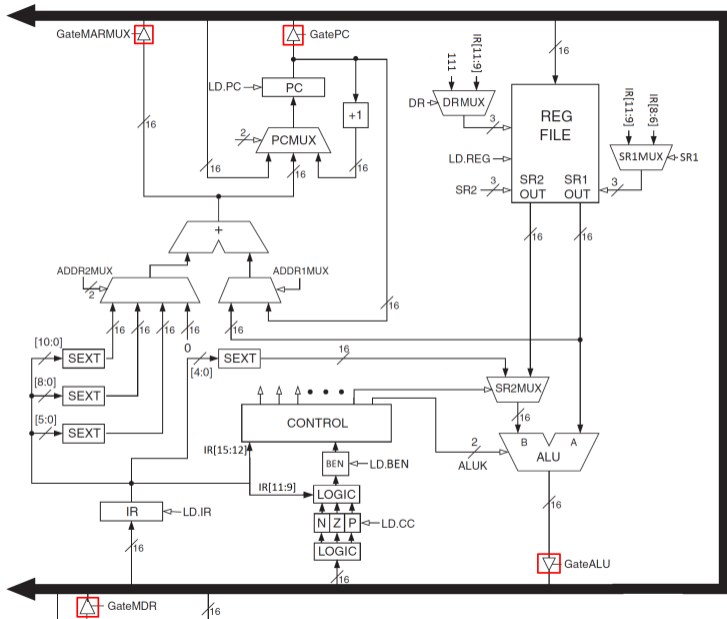

Questions?



The computer looked normal size for a black space-borne computer satellite — about a thousand miles across.

— DOUGLAS ADAMS (1979)

